

# Lógica e Sistemas Digitais

Dados e Controlo microprogramado

João Pedro Patriarca ([jpatri@cc.isel.ipl.pt](mailto:jpatri@cc.isel.ipl.pt))


Slides inspirados nos slides do prof. Mário Véstias


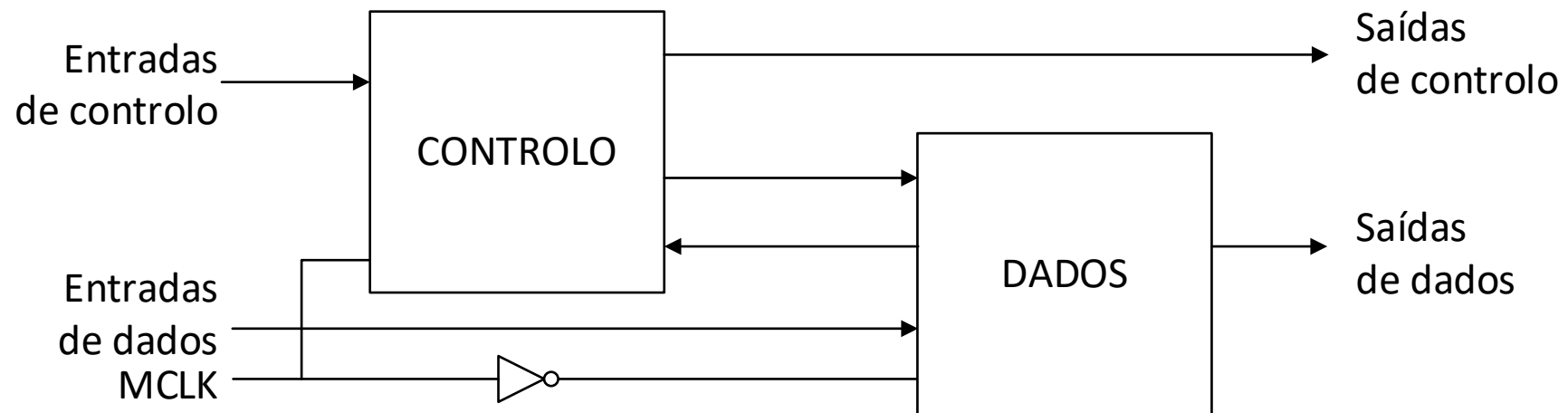
# Circuito de dados e controlo


---

- Dois circuitos principais
  - Circuito de controlo ou módulo de controlo
  - Circuito de dados ou módulos funcionais



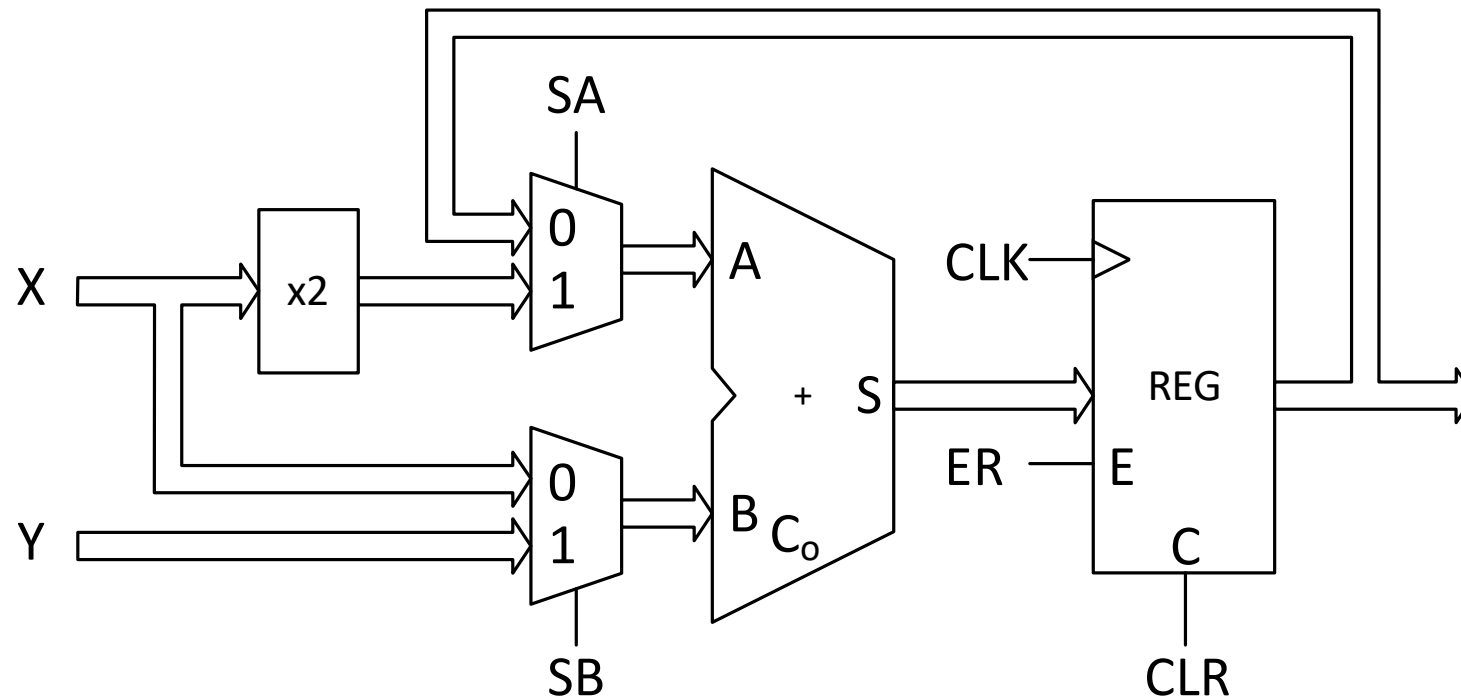
# Exemplo – recursos para realizar a operação $R = 3X + Y$

- Processo para produzir o resultado  $3X + Y$ 
  1.  $\text{Temp1} = 2 * X + X$
  2.  $R = \text{Temp1} + Y$



 
# Exemplo – flag de erro

- Produz uma *flag* que fica ativa em caso de resultado com erro
- Processo para produzir a *flag* de erro
  1. Erro se  $2 * X$  produzir arrasto
  2. Erro se  $2 * X + X$  produzir arrasto
  3. Erro se  $\text{Temp1} + Y$  produzir arrasto




# Exemplo – circuito de dados completo

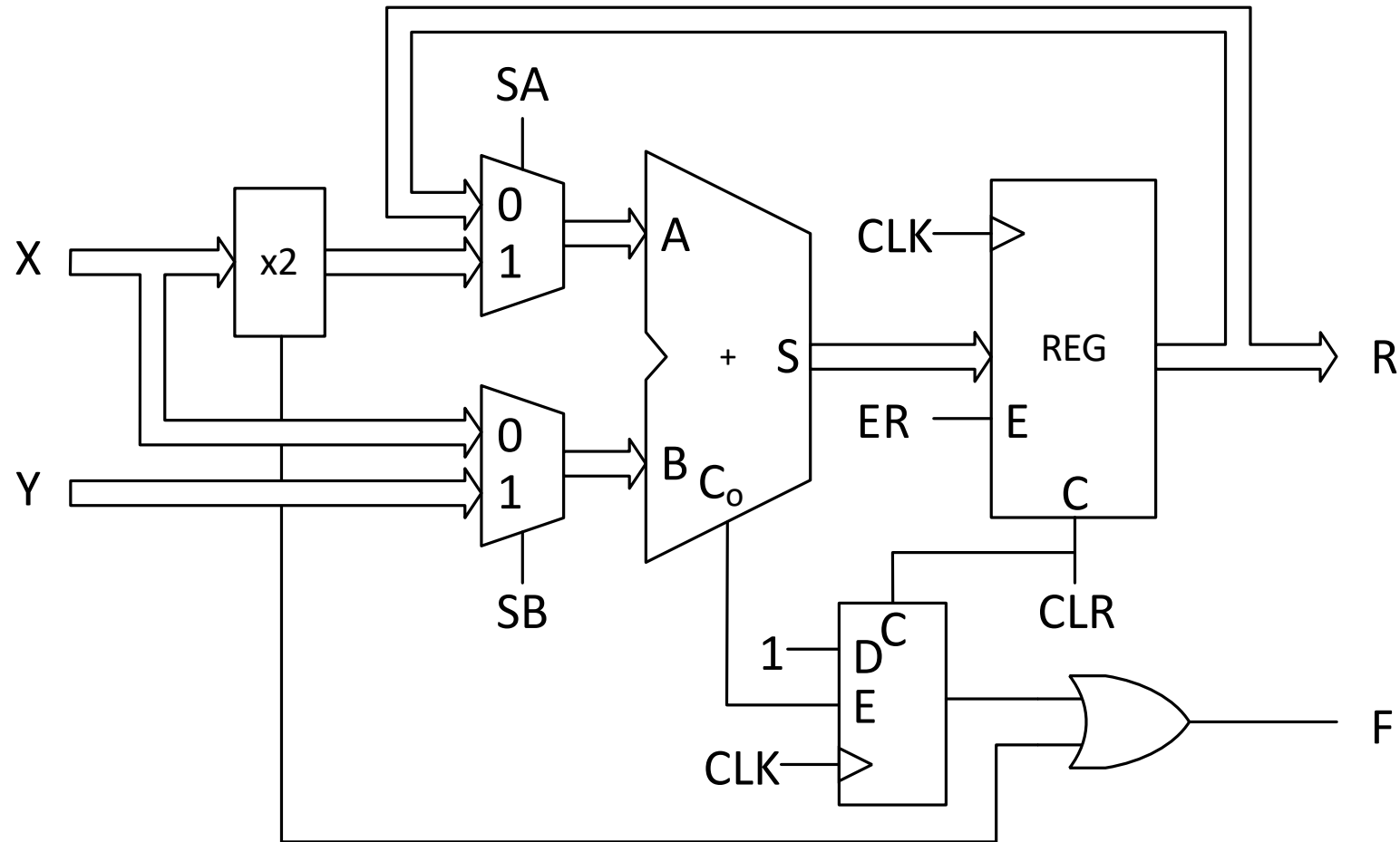

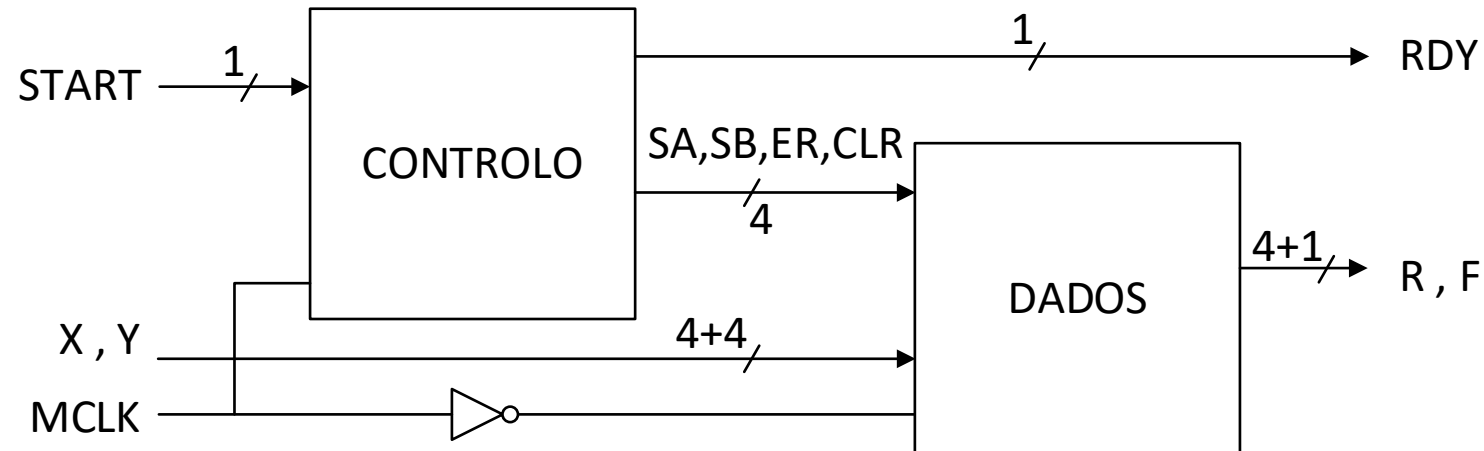
# Exemplo – circuito de dados e controlo


- Entrada START para indicar início de operação
- Mantém último resultado enquanto START ativo
- Saída RDY para indicar resultado produzido
- *Clock* do controlo e dados a funcionar com o mesmo período e em oposição de fase



# Exemplo – sistema de controlo

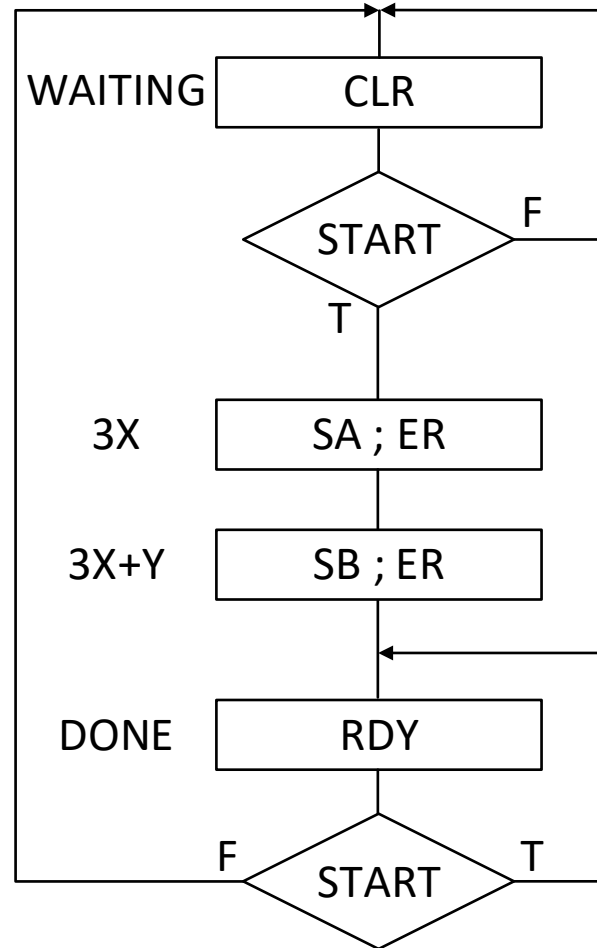

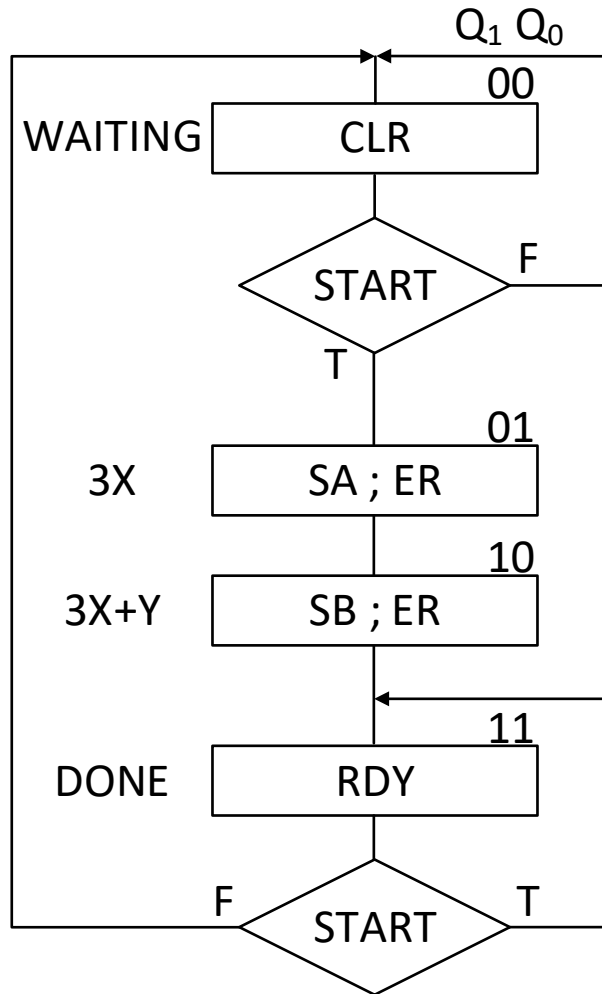
# Exemplo – sistema de controlo – tabela de transição de estados e saídas



EP		Ent.	ES		Saídas				
$Q_1$	$Q_0$		$Q_1 + 1$	$Q_0 + 1$	CLR	ER	SB	SA	RDY
0	0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	0	0	0
0	1	-	1	0	0	1	0	1	0
1	0	-	1	1	0	1	1	0	0
1	1	0	0	0	0	0	0	0	1
1	1	1	1	1	0	0	0	0	1


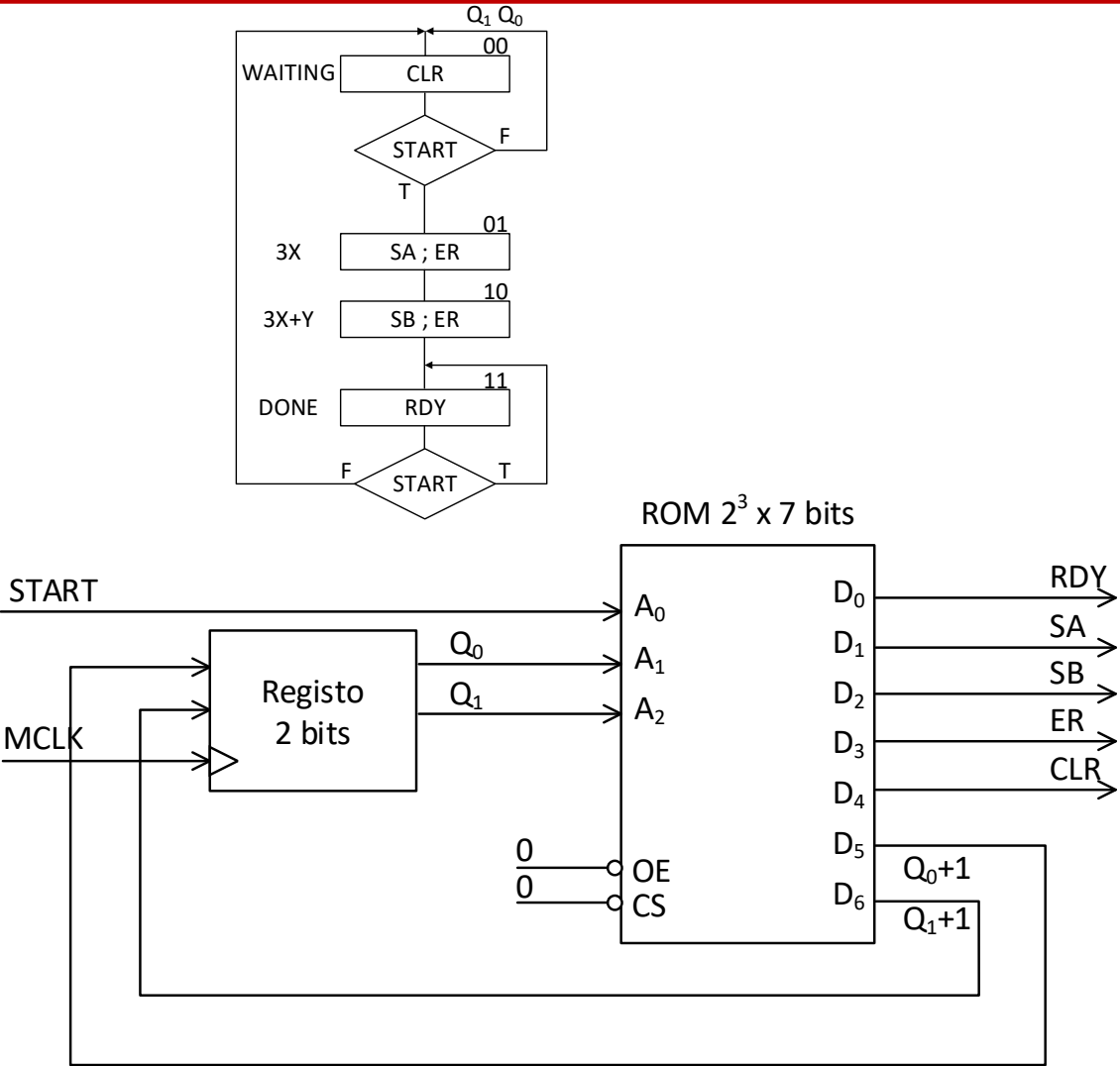
# Exemplo – sistema de controlo – controlo microprogramado



Endereços			Dados						
A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
Q <sub>1</sub>	Q <sub>0</sub>	START	Q <sub>1</sub> + 1	Q <sub>0</sub> + 1	CLR	ER	SB	SA	RDY
0	0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	0	0	0
0	1	0	1	0	0	1	0	1	0
0	1	1	1	0	0	1	0	1	0
1	0	0	1	1	0	1	1	0	0
1	0	1	1	1	0	1	1	0	0
1	1	0	0	0	0	0	0	0	1
1	1	1	1	1	0	0	0	0	1

# Exemplo – VHDL da entidade de topo (1 de 2)

```
entity X3_PLUS_Y is port(  
    RESET: in std_logic;  
    MCLK: in std_logic;  
    START: in std_logic;  
    X,Y: in std_logic_vector(3 downto 0);  
    R: out std_logic_vector(3 downto 0);  
    RDY, F: out std_logic);  
end entity;  
  
architecture X3_PLUS_Y_ARCH of X3_PLUS_Y is  
  
    component X3_PLUS_Y_CONTROL port(  
        RST, CLK: in std_logic;  
        START: in std_logic;  
        CLR, ER, SA, SB, RDY: out std_logic);  
    end component;  
  
    component X3_PLUS_Y_DATA port(  
        CLK: in std_logic;  
        X,Y: in std_logic_vector(3 downto 0);  
        CLR, ER, SA, SB: in std_logic;  
        R: out std_logic_vector(3 downto 0);  
        F: out std_logic);  
    end component;  
  
    signal N_MCLK: std_logic;  
    signal CLR_LK, ER_LK, SA_LK, SB_LK: std_logic;
```

# Exemplo – VHDL da entidade de topo (2 de 2)

---

```
begin
  N_MCLK <= not MCLK;

  CONTROL: X3_PLUS_Y_CONTROL port map(RST => RESET,
    CLK => MCLK, START => START, CLR => CLR_LK,
    ER => ER_LK, SA => SA_LK, SB => SB_LK, RDY => RDY);
  DATA: X3_PLUS_Y_DATA port map(CLK => N_MCLK,
    X => X, Y => Y, CLR => CLR_LK, ER => ER_LK,
    SA => SA_LK, SB => SB_LK, R => R, F => F);
end architecture;
```

# Exemplo – VHDL da entidade de controlo (1 de 2)

---

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity X3_PLUS_Y_CONTROL is port(
    RST, CLK: in std_logic;
    START: in std_logic;
    CLR, ER, SA, SB, RDY: out std_logic);
end entity;

architecture X3_PLUS_Y_CONTROL_ARCH of X3_PLUS_Y_CONTROL is

    type ROM_type is array (0 to 7) of std_logic_vector(6 downto 0);

    constant ROM: ROM_type := (0  => "0010000",
                                1  => "0110000",
                                2  => "1001010",
                                3  => "1001010",
                                4  => "1101100",
                                5  => "1101100",
                                6  => "0000001",
                                7  => "1100001");
```

## Exemplo – VHDL da entidade de controlo (2 de 2)

```
component FFD
port( CLK : in std_logic;
      RESET : in STD_LOGIC;
      SET : in std_logic;
      D : IN STD_LOGIC;
      EN : IN STD_LOGIC;
      Q : out std_logic
    );
end component;

signal ADDR: std_logic_vector (2 downto 0);
signal DATA: std_logic_vector (6 downto 0);
signal PS: std_logic_vector (1 downto 0);

begin

  UX0: FFD port map (CLK => CLK, RESET => RST, SET => '0', D => DATA(5), EN => '1', Q => PS(0));
  UX1: FFD port map (CLK => CLK, RESET => RST, SET => '0', D => DATA(6), EN => '1', Q => PS(1));
  ADDR <= PS(1) & PS(0) & START;
  DATA <= ROM( to_integer(unsigned(ADDR)));
  CLR <= DATA(4);
  ER <= DATA(3);
  SB <= DATA(2);
  SA <= DATA(1);
  RDY <= DATA(0);

end architecture;
```

# Exemplo – VHDL da entidade de dados (1 de 3)

```
entity X3_PLUS_Y_DATA is port(  
    CLK: in std_logic;  
    X,Y: in std_logic_vector(3 downto 0);  
    CLR, ER, SA, SB: in std_logic;  
    R: out std_logic_vector(3 downto 0);  
    F: out std_logic);  
end entity;  
  
architecture X3_PLUS_Y_DATA_ARCH of X3_PLUS_Y_DATA is  
  
    component REG4_W_EN_CL port (  
        CLK: in std_logic;  
        D: in std_logic_vector(3 downto 0);  
        EN, CL: in std_logic;  
        Q: out std_logic_vector(3 downto 0));  
    end component;  
  
    component FFD port(  
        CLK : in std_logic;  
        RESET : in STD_LOGIC;  
        SET : in std_logic;  
        D : IN STD_LOGIC;  
        EN : IN STD_LOGIC;  
        Q : out std_logic);  
    end component;
```

## Exemplo – VHDL da entidade de dados (2 de 3)

---

```
component DOUBLE4 port(  
    A : in std_logic_vector(3 downto 0);  
    O : out std_logic_vector(3 downto 0);  
    Cy: out std_logic);  
end component;  
  
component ADDER4 port(  
    A, B: in std_logic_vector(3 downto 0);  
    Ci: in std_logic;  
    S: out std_logic_vector(3 downto 0);  
    Co: out std_logic);  
end component;  
  
component MUX2X1_4 port(  
    I0, I1: in std_logic_vector(3 downto 0);  
    S: in std_logic;  
    Y: out std_logic_vector(3 downto 0));  
end component;  
  
signal DOUBLE_LK, A_LK, B_LK, S_LK, R_LK: std_logic_vector(3 downto 0);  
signal DOUBLE_CO_LK, C4_LK, C4R_LK: std_logic;
```

# Exemplo – VHDL da entidade de dados (3 de 3)

---

begin

```
U0: DOUBLE4 port map (A => X, O => DOUBLE_LK, Cy => DOUBLE_CO_LK);
U1: MUX2X1_4 port map (I0 => R_LK, I1 => DOUBLE_LK, S => SA, Y => A_LK);
U2: MUX2X1_4 port map (I0 => X, I1 => Y, S => SB, Y => B_LK);
U3: ADDER4 port map (A => A_LK, B => B_LK, S => S_LK, Ci => '0', Co => C4_LK);
U4: FFD port map (CLK => CLK, RESET => CLR, SET => '0', D => '1', EN => C4_LK, Q => C4R_LK);
U5: REG4_W_EN_CL port map (CLK => CLK, D => S_LK, EN => ER, CL => CLR, Q => R_LK);

R <= R_LK;
F <= DOUBLE_CO_LK or C4R_LK;
```

end architecture;